
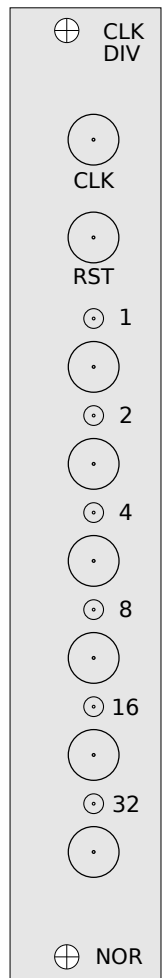


CLOCK DIVIDER

mix of two very similar schematics:

Rönneberg and Kristian Blasol (MiaW)
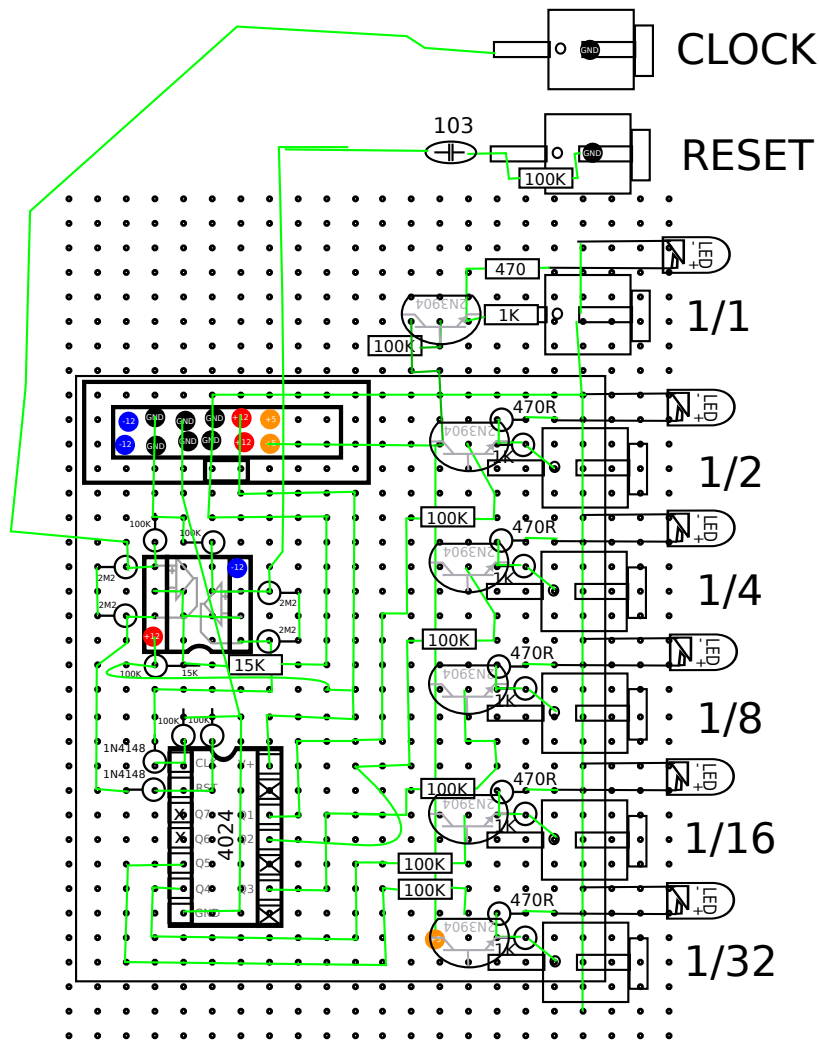
<http://familienronnberg.se/~niklas/diy/eurorack/divider/>




TL072 x1
4024 x1
2N3904 x1
1N4148 x1


caps
10n x1

resistors
470R x6
1K x6
15K x2
100K x13
2M2 x4


BC550 Transistor Pinout

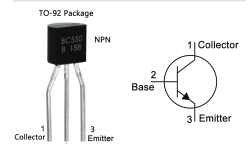

more or less the same as 2N3904

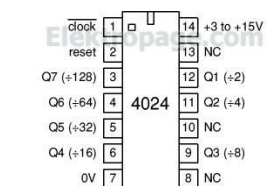

Divider
Niklas Rönneberg

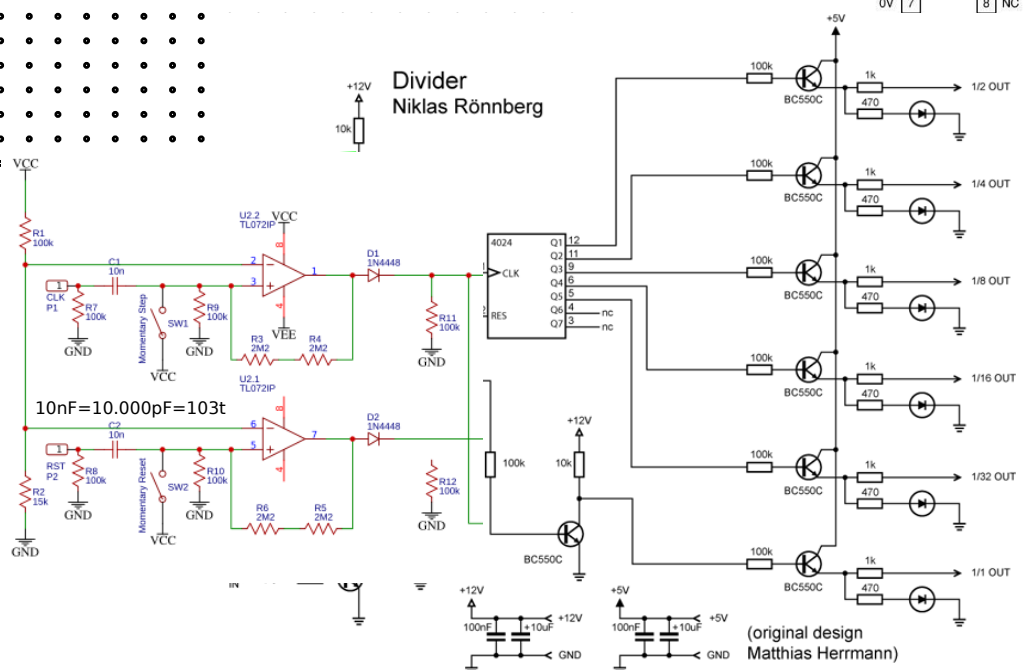

(original design
Matthias Herrmann)