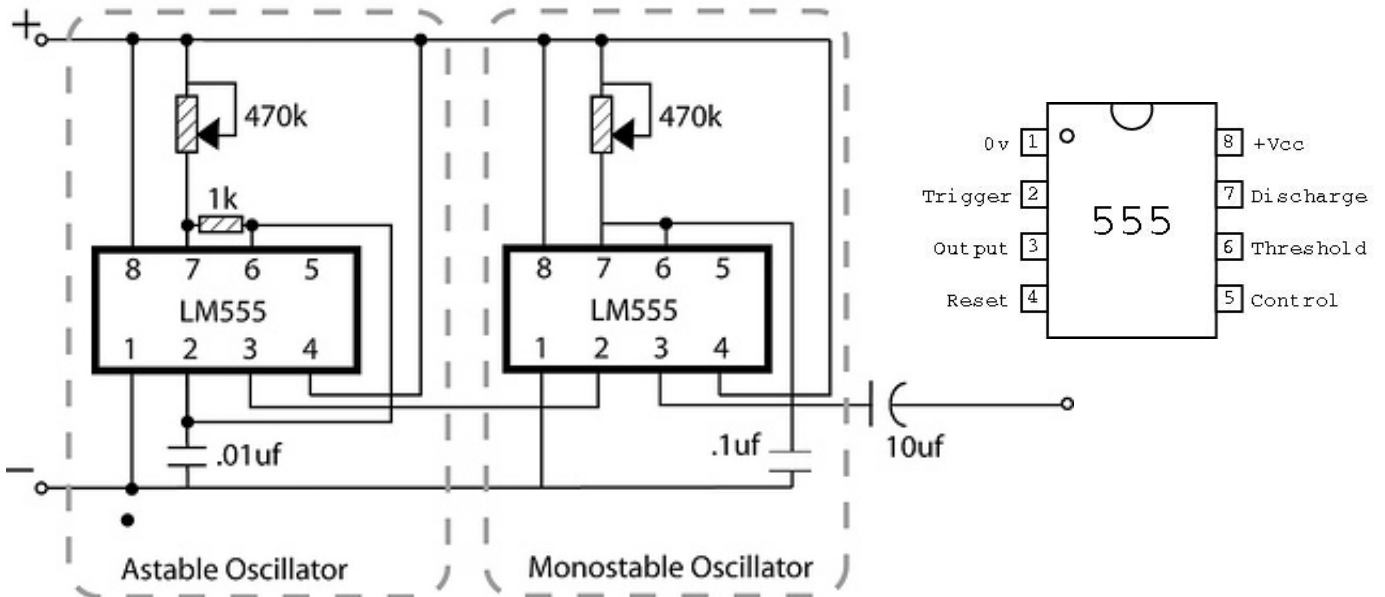


Stepped Tone Generator - Aka the Atari Punk Console



atari punk console composed as two 555s. Its basically an astable Oscillator driving a Monostable Oscillator.

www.robthefiddler.com

Original circuit Forrest M. Mims, III (Siliconcepts, 1984)

